

# Series LC Circuit Worksheet

## Introduction

Understanding the behavior of reactive components such as capacitors and inductors based on their complex impedances is a critical skill in electrical engineering. In this lesson we will analyze the behavior of one such circuit using Laplace transforms.

## Discussion Overview

As discussed in the lecture, LC circuits tend to oscillate at certain frequencies determined by the combination of the capacitor's and inductor's impedances. To better understand the frequency response of such circuits, we will examine the following circuit.

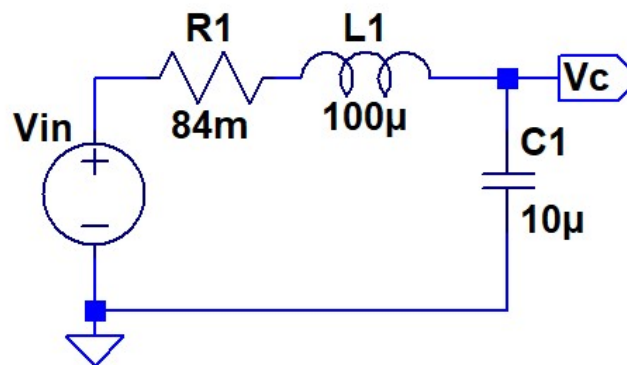


Figure 1 - Series LC Circuit

In order to determine the voltage  $V_C$  across the capacitor, we use the voltage divider equation using the impedances of  $R_1$ ,  $L_1$  and  $C_1$ . Note that resistor  $R_1$  represents the series resistance of the inductor; and otherwise,  $L_1$  is treated as an ideal inductor while  $C_1$  is treated as an ideal capacitor. Therefore,

$$V_C = V_{in} \frac{\frac{1}{sC}}{\frac{1}{sC} + R + sL} = V_{in} \frac{1}{1 + sCR + s^2CL}$$

To examine the behavior of the circuit in frequency domain, we let  $s = j\omega$ :

$$V_C = V_{in} \frac{1}{1 + j\omega CR - \omega^2 CL} = V_{in} \frac{1}{1 - \omega^2 CL + j\omega CR}$$

The magnitude of the voltage across the capacitor is, therefore, given by

$$|V_C| = \left| V_{in} \frac{1}{1 - \omega^2 CL + j\omega CR} \right| = V_{in} \frac{1}{\sqrt{(1 - \omega^2 CL)^2 + (\omega CR)^2}} \quad \text{Eq. 1}$$

As seen in Eq. 1,  $V_C$  is a function of frequency  $\omega$  ( $= 2\pi f$ ). We will now examine how  $V_C$  changes as a function of frequency. This is called the frequency response of the circuit.

## Frequency Response

We will examine Eq. 1 for three different regions in frequency domain; low frequencies, high frequencies and the so called “corner frequency”.

### Low Frequencies

First, we note that for lower frequencies close to zero, the denominator in Eq. 1 is approximately 1. Therefore, for lower frequencies, the voltage across the capacitor is approximately the same as the input voltage:

$$V_C|_{\omega \rightarrow 0} \approx V_{in}$$

We note that this behavior is in line with our expectations for very low frequency signals including DC. For low frequencies, an inductor acts like a short while a capacitor acts like an open circuit which would lead to  $V_C = V_{in}$ .

### High Frequencies

The second region of interest is for very large frequencies. For large frequencies, the denominator in Eq. 1 is dominated by  $\omega$ , and as  $\omega$  gets larger, the fraction goes to zero. Therefore, for large frequencies, the voltage across the capacitor tends towards zero:

$$V_C|_{\omega \rightarrow \infty} \approx 0$$

This behavior, again, is in line with our expectations. For large frequencies, an inductor acts like an open while a capacitor acts like a short leading to  $V_C = 0$ .

### Corner Frequency

The final region of interest is around the frequency  $\omega = \frac{1}{\sqrt{LC}}$ . Assuming that  $R$  is fairly small, the denominator in Eq. 1 is dominated by the term  $(1 - \omega^2 CL)$ . For  $\omega = \frac{1}{\sqrt{LC}}$ , this term is equal to zero which would lead to a very large value for the fraction in Eq. 1. We can find the exact value of  $V_C$  by plugging  $\omega = \frac{1}{\sqrt{LC}}$  in Eq. 1:

$$V_C|_{\omega = \frac{1}{\sqrt{LC}}} = V_{in} \frac{1}{R} \sqrt{\frac{L}{C}}$$

Name: \_\_\_\_\_

The plot in Figure 2 shows the frequency response of the circuit in Figure 1 assuming  $V_{in} = 1$ . For the R, L and C values in Eq. 1:

$$f = \frac{\omega}{2\pi} = \frac{1}{2\pi\sqrt{LC}} = 5.03\text{KHz}$$

Eq. 2

and

$$V_C|_{\omega=\frac{1}{\sqrt{LC}}} = V_{in} \frac{1}{R} \sqrt{\frac{L}{C}} \approx 31.5\text{dB}$$

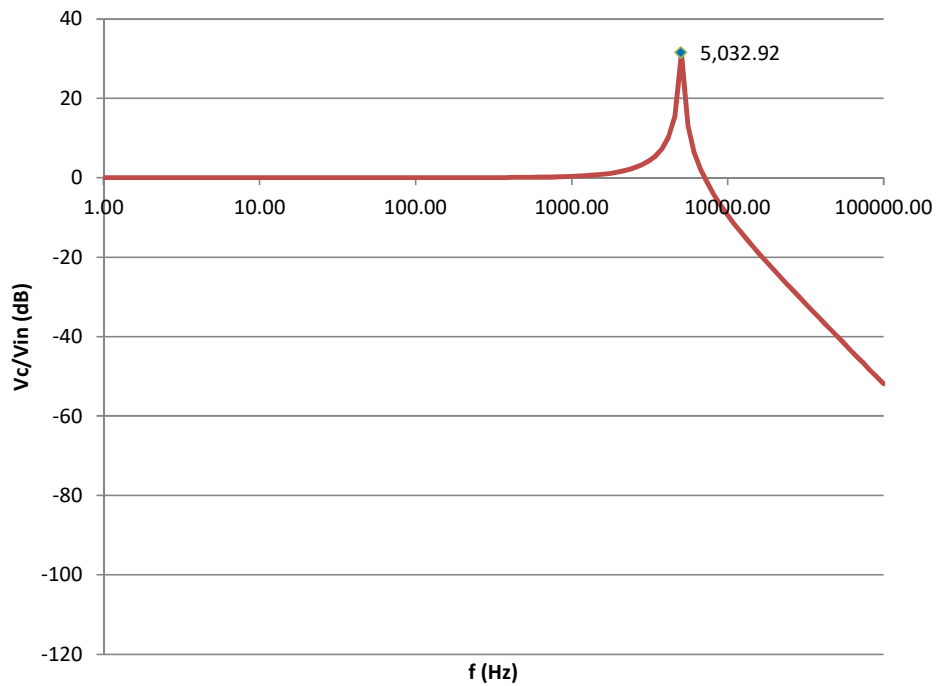


Figure 2 - Frequency Response of an LC Circuit

## Procedure

In this section, you are asked to create a SPICE model and also build the circuit in Figure 3. Note that the series resistance of the inductor will be specified as part of the inductor's parameters.

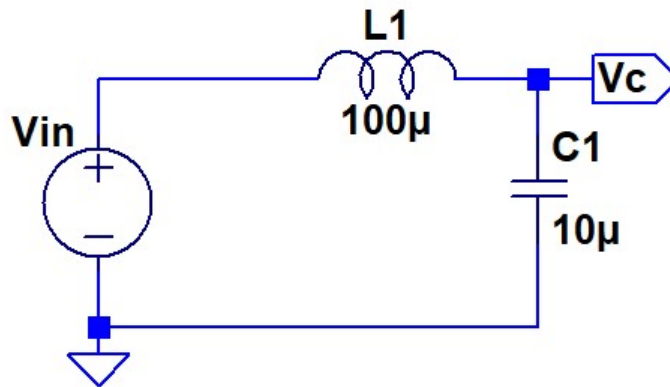


Figure 3 - LTSpice LC Circuit

## LTSpice Model

- Capture the circuit in Figure 3 in LTSpice.
- When selecting a value for L1, chose the part shown below.

Select Stock Inductor				
<div>Quit and Edit Database</div> <div>List All Inductors in Database</div> <div>OK</div> <div>Cancel</div>				
L[μH]	Mfg.	Part No.	Ipk[A]	Rser[Ω]
100.0	Coilcraft	RFS1412-104	2.600	0.083
100.0	Würth Elektronik	7447221101 WE-TIF 1016	2.600	0.080
100.0	Coilcraft	PCH-45X-104	2.800	0.074
100.0	Würth Elektronik	7447231101 WE-TIF 1018	2.800	0.072
100.0	Gowanda	059AT1003V	3.000	0.050
100.0	Gowanda	894AT1003V	3.000	0.030
100.0	Coilcraft	PCV-1-104-03	3.400	0.058
100.0	Gowanda	GT10-108	3.500	0.040

*Note that selecting this part, sets the inductor's series resistance to 83mΩ*

- Set your voltage source to a "PULSE" source with the following parameters
  - Initial voltage = 0
  - Von = 1V
  - Delay = 0

Name: \_\_\_\_\_

- d. Rise time =  $1\mu\text{s}$
- e. Fall time =  $1\mu\text{s}$
- f. On time =  $3.179\text{ms}$
- g. Period =  $6.358\text{ms}$

- D. Setup the model to run a “transient” simulation with the following parameters
- a. Starting the print at time 0,
  - b. Ending at time  $3.179\text{ms}$ ,
  - c. Starting capture at time 0,
  - d. With a maximum simulation step size of  $1\mu\text{s}$ , and
  - e. Setting the external voltage sources to 0 at the “startup”

*Below is the syntax for your reference:*

`.tran <Tprint> <Tstop> [<Tstart> [<Tmaxstep>]] [<options>]`

- E. Run the simulation and display the waveform for the voltage  $V_c$ .
- F. What does the waveform look like?


- G. Estimate the frequency of the waveform and record it here

$f = \text{_____} \text{Hz}$

## Frequency Response

In this section, we will use the FFT tool of LTSpice to plot the frequency response of the voltage across the capacitor. FFT stands for Fast Fourier Transform, and it is a mathematical algorithm for extracting the various frequency components present in a signal. ( The details of the FFT algorithm are beyond the scope of this level.)

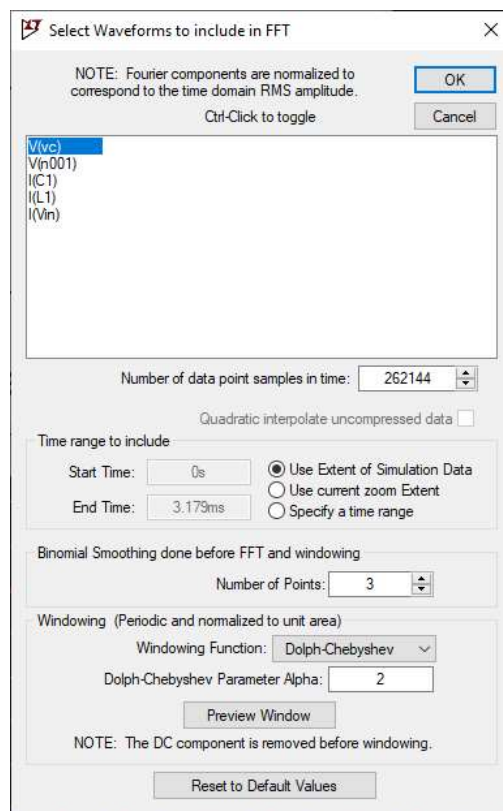- H. Right click on the waveform window and select View → FFT
- I. From the FFT window, select V(vc) to display
- J. Leave all the settings as default except for the following:
  - a. Set the “Windowing Function” to “Dolph-Chebyshev”, and
  - b. Set the “Dolph-Chebyshev Parameter Alpha” to 2.



- K. Select to run the FFT.

*You should now see a waveform similar to the one given in Figure 2.*

Name: \_\_\_\_\_

- L. Measure the frequency at which the response peaks and record it below.

$$f = \text{_____} Hz$$

How does this value compare with the calculated value in Eq. 2 or the estimated value in step G?

### Lab Build and Measurements

In this section, you are asked to build the circuit in Figure 3 and make measurements using an oscilloscope.

- A. Note the values of your inductor and capacitor and record them here

$$C = \text{_____} F$$

$$L = \text{_____} H$$

- B. Measure the series resistance of the inductor and record it here

$$R_L = \text{_____} \Omega$$

- C. Build the circuit in Figure 3 on a breadboard.

- D. Set the waveform generator on your oscilloscope to a square wave with the following parameters:

- Amplitude = 0.5V ( $V_{pk-pk} = 1V$ )
- Offset = 0.5V
- Frequency = 160Hz

- E. Use the waveform generator as the input source to your circuit.

- F. Connect the oscilloscope to observe the voltage across your capacitor. Here are the suggested initial settings:

- Ch. 1 volts/div = 0.5V
- Horizontal sec/div = 2ms
- Trigger set to the leftmost location on the screen (~16ms)

Name: \_\_\_\_\_

G. What does the waveform look like?

H. Estimate the frequency of the waveform and record it here

$f =$  \_\_\_\_\_  $Hz$

I. Use the “Math” function to plot the FFT of the signal.

J. Measure the frequency at which the response peaks and record it below.

$f =$  \_\_\_\_\_  $Hz$

How does this value compare with the calculated value in Eq. 2 or the estimated value in step J above?