

Simple Thermal-Sensor Circuit

Discussion Overview

The basics of circuit design include identifying the required voltages and currents of active components used in a circuit and adjusting passive component values to achieve the desired voltages and currents.

For our simple thermo-resistor circuit, our active component is an LED (Light Emitting Diode) and a transistor combination which we will treat as a “black box”¹. We will use the specs (specifications) for this black box circuit to determine the voltage required to turn on the LED when the temperature detected by the sensor drops below a certain amount.

We will also use a thermo-resistor as our sensor. The specs for the thermo-resistor will come from our last experiment; namely the resistance of the thermo-resistor in ambient and low temperatures.

Schematics

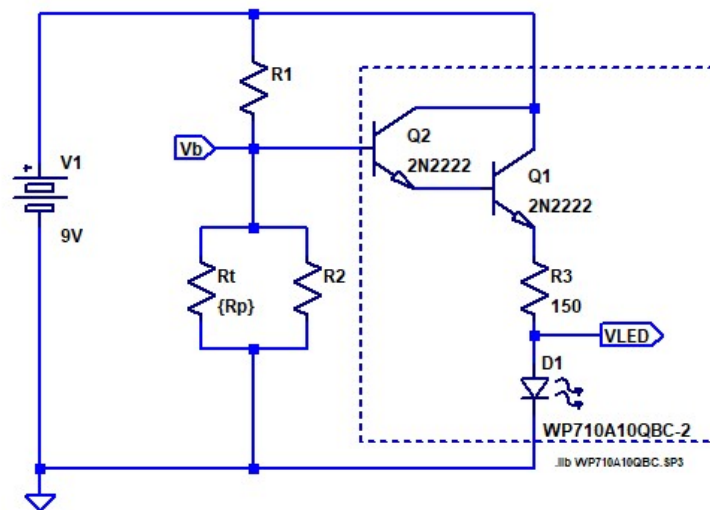


Figure 1 – Simple Thermo-detector Circuit

Note that the black box circuit in the schematics above is marked by the dashed rectangle. The followings are the specs for the black box:

- $V_b = 3V$ for the LED to turn on

¹ A “black box” is usually referred to a circuit where we don’t know (or need to know) the details of the circuit as long as we know the required voltages and currents for input and output ports.

b) $V_b \leq 4.5V$ for all values of R_t

Procedure

First, let's look at the equivalent resistance for the parallel sub-circuit in in Figure 1. This equivalent circuit is shown below:

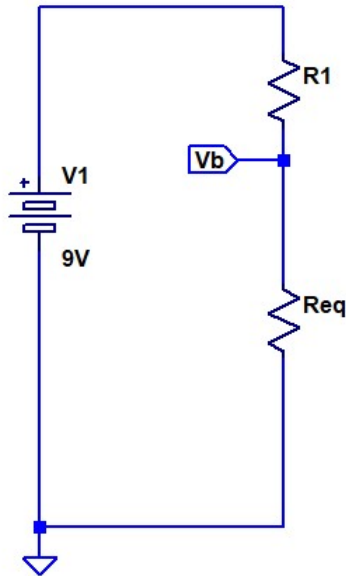


Figure 2 – Equivalent Resistor Network

The circuit in Figure 2 is now a simple series resistor network or a voltage divider circuit. Recall that for a series resistor network, the voltage across each resistor is proportional to the ratio of the value of that resistor to the total resistance. In the case of Figure 2:

$$V_b = V_{batt} \frac{R_{eq}}{R_1 + R_{eq}} \quad \text{Eq. 1}$$

From our design requirement (b), we know that $V_b \leq 4.5V$. Therefore, the ratio

$$\frac{R_{eq}}{R_1 + R_{eq}} \leq \frac{1}{2}$$

This can be achieved by setting $R_{eq} = R_1$.

Now, examining R_{eq} by itself, we note that in a parallel resistor network,

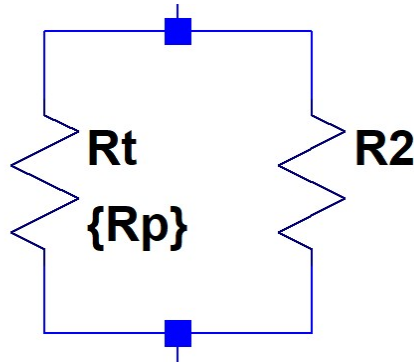


Figure 3 – Parallel Resistor Sub-Circuit

the equivalent resistance of the network can never be larger than the smallest resistor in the network. Therefore, by setting $R_2 = R_1$, we ensure that no matter how large the value of R_t is, the value of R_{eq} is never larger than R_1 , and consequently, $\frac{R_{eq}}{R_1 + R_{eq}}$ for the series circuit in Figure 2 will never be larger than $\frac{1}{2}$.

Therefore, the circuit of Figure 1 will now be as shown below.

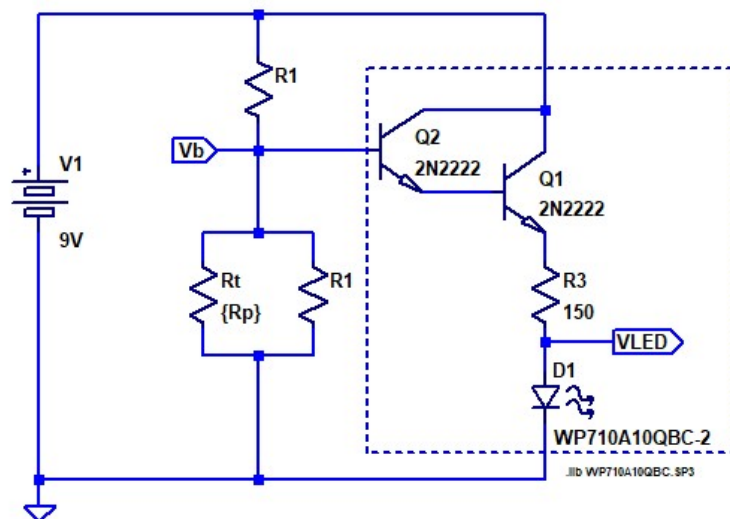


Figure 4 – Simple Thermo-detector Circuit with $R_2 = R_1$

Now, in order to determine the value of R_1 , we will use our design requirement (a) and the following steps.

- A. Design requirement (a) states that $V_b = 3V$ for LED to turn on. Referring to Figure 2 and Eq. 1:

$$4 = V_{batt} \frac{R_{eq}}{R_1 + R_{eq}}$$

However, $V_{batt} = 9$.

$$3 = 9 \frac{R_{eq}}{R_1 + R_{eq}}$$

B. Solving above equation for R_{eq} , we have

$$R_{eq} = \frac{3}{6} R_1 = \frac{1}{2} R_1$$

C. R_{eq} for the parallel resistor sub-circuit, on the other hand, is given by

$$R_{eq} = \frac{R_1 R_t}{R_1 + R_t}$$

Setting this equation equal to the one in step B:

$$\frac{R_1 R_t}{R_1 + R_t} = \frac{1}{2} R_1$$

and solving for R_1 , we have

$$R_1 = R_t$$

D. Now, by looking at our data collected for R_t for ambient and “cold” temperatures, we can pick a value to plug in for R_t to get a value for R_1 . Write your selected value for R_t and R_1 below.

$$R_t = \underline{\hspace{2cm}}$$

$$R_1 = \underline{\hspace{2cm}}$$

Simulation

In real practice, once a design is completed on paper, engineers try to simulate the circuit to detect and correct any possible mistakes in the design.

- A. Capture the schematic for your design in LTSpice. Your final schematic should look like the one below. Make sure to include and select the correct library for the LED D1.

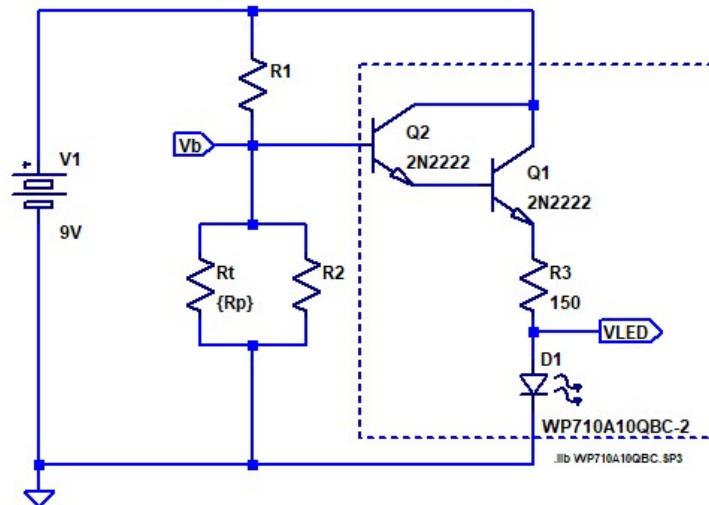


Figure 5 - LTSpice Simulation Circuit

- B. Simulate your design for values of R_t ranging from 80K to 800K to make sure the circuit is behaving as you expect it. From the simulation results, collect the values for V_b in the table below for the different values of R_t indicated.

R_t	V_b
100K	
140K	
200K	
220K	
240K	
800K	

Name: _____

Build

Build your circuit from Figure 5 on a breadboard. Measure the voltage at V_b with respect to ground for when the LED is off and when the LED is on. Record the values below.

V_b for LED Off = _____

V_b for LED On = _____